

HW #2: Instruction Decoder



國立陽明交通大學
NATIONAL YANG MING CHIAO TUNG UNIVERSITY

Chun-Jen Tsai
NYCU
03/18/2024


HW 2: Instruction Decoder

- ❑ Goal: design a MIPS instruction decoder
 - The input to the decoder is a 32-bit MIPS instruction
 - The output to the decoder should be connected to the register file and the ALU for computation

- ❑ The deadline of the lab is on 4/04, by 5:00pm.

The Top-Level Block Diagram

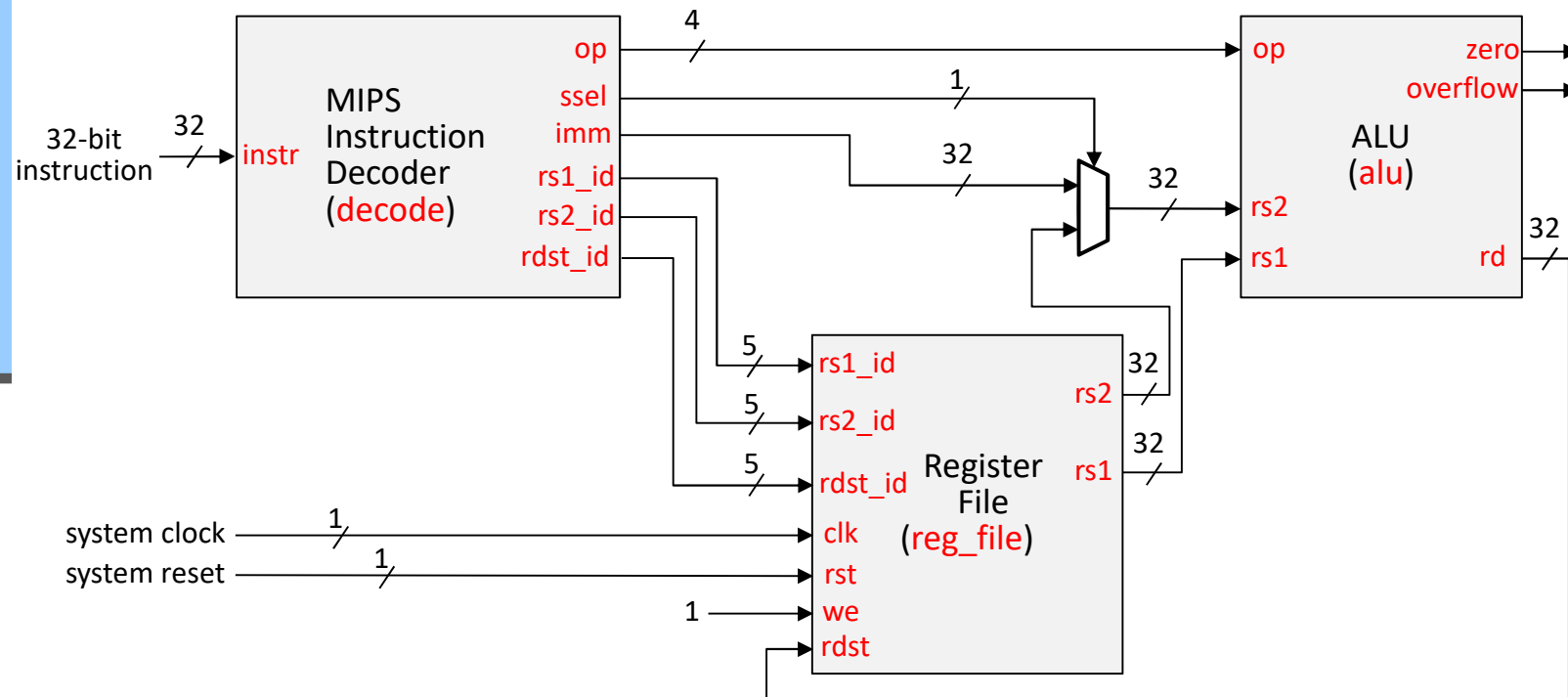- ❑ The block diagram of the system is as follows:
 - Note that your declarations must use the module & port names in red precisely; the bit-width must be the same as well
 - The immediate value (**imm**) must be sign-extended to 32-bit



The Instruction Decoder

- ❑ Your instruction decoder must decode the following instructions
 - The complete MIPS instructions are shown in the file `MIPS_ISA_Sheet.pdf`

Assembly instruction	Function	Format	opcode	funct
<code>add rd, rs, rt</code>	addition: $rd \leftarrow rs + rt$	R	0x00	0x20
<code>addi rt, rs, imm</code>	add immediate: $rt \leftarrow rs + imm$	I	0x08	0x00
<code>sub rd, rs, rt</code>	subtraction: $rd \leftarrow rs - rt$	R	0x00	0x22
<code>and rd, rs, rt</code>	$rd \leftarrow rs \text{ and } rt$	R	0x00	0x24
<code>or rd, rs, rt</code>	$rd \leftarrow rs \text{ or } rt$	R	0x00	0x25
<code>nor rd, rs, rt</code>	$rd \leftarrow \sim(rs \text{ or } rt)$	R	0x00	0x27
<code>slt rd, rs, rt</code>	$rd \leftarrow (rs < rt) ? 32'h1 : 32'h0;$	R	0x00	0x2a
<code>slti rt, rs, imm</code>	$rt \leftarrow (rs < imm) ? 32'h1 : 32'h0;$	I	0x0a	0x00

A Design Flaw in the MIPS ISA

- ❑ Note that for MIPS, there is a design flaw in the instruction format:
 - The name for the destination register is not consistent: for different instructions, it can be either `rd` or `rt`!
 - This design flaw has been corrected in the RISC-V ISA, where `rd` is used universally as the target register
- ❑ Therefore, the output port `rdst_id` of the decode module may be the ID for `rd` or `rt`, depending on the instructions

Port Definitions of decode Module

- ❑ The decode module is a combinational circuit with the I/O ports defined as follows:

```
module decode #(parameter DWIDTH = 32)
(
    input  [DWIDTH-1:0] instr, // Input instruction.

    output [3 : 0]      op,      // Operation code for the ALU.
    output              ssel,    // Select the signal for either
                                // the immediate value or rs2.

    output [DWIDTH-1:0] imm,      // The immediate value (if used).
    output [4 : 0]      rs1_id,   // register ID for rs.
    output [4 : 0]      rs2_id,   // register ID for rt (if used).
    output [4 : 0]      rdst_id,  // register ID for rd or rt (if used).
);
```

Declaration of `reg_file` Module

- ❑ The register file module contains 32 32-bit registers:

```
module reg_file #(parameter DWIDTH = 32)
(
    input                clk, // system clock
    input                rst, // system reset

    input  [4 : 0]       rs1_id, // register ID of data #1
    input  [4 : 0]       rs2_id, // register ID of data #2 (if any)

    input                we,      // if (we) R[rdst_id] ← rdst
    input  [4 : 0]       rdst_id, // destination register ID
    input  [DWIDTH-1 : 0] rdst,    // input to destination register

    output [DWIDTH-1 : 0] rs1, // register operand #1
    output [DWIDTH-1 : 0] rs2  // register operand #2 (if any)
);

reg [DWIDTH-1:0] R[0:31];

. . . (You must finish the rest of the code) . . .
```

The Register File Behavior

- ❑ The register file is a sequential module that updates the register array at positive edges of the clock signal
 - Register 0 is a read-only register of the value 32'h0
 - All the registers shall be initialized to all zeros upon reset
- ❑ It has two read ports and one write port (`rdst`)
 - Read ports (`rs1`, `rs2`) are combinational output of the data
 - Write port stores the data into one of the registers when the write enable (`we`) signal is 1 at every positive clock edge
 - For this HW, `we` is always connected to 1 since we assume one instruction will be executed at every clock cycle

HW 2 Guidelines

- ❑ You should upload all your code to E3 before the deadline
- ❑ The sample package, `HW2_sample_tb.tgz`, contains sample testbench files and the templates of `decode.v` and `reg_file.v`. **Please read `readme.txt` in that package carefully!**
- ❑ For grading, TAs will use a more thorough testbench